

RADIO RECEIVER CIRCUITS

Handbook
by

E. M. SQUIRE

CONTAINING PRACTICAL NOTES ON THE
OPERATION OF BASIC MODERN
SUPERHETERODYNE AND STRAIGHT CIRCUITS

P I T M A N

RADIO RECEIVER CIRCUITS HANDBOOK

CONTAINING PRACTICAL NOTES ON THE
OPERATION OF BASIC MODERN
SUPERHETERODYNE AND STRAIGHT
CIRCUITS

BY
E. M. SQUIRE

THIRD EDITION



LONDON
SIR ISAAC PITMAN & SONS, LTD.
1946

CONTENTS

CHAP.		PAGE
	PREFACE	v
I.	HIGH-FREQUENCY AMPLIFIERS	1
II.	FREQUENCY CHANGER CIRCUITS	23
III.	DETECTORS	39
IV.	LOW-FREQUENCY AMPLIFIER CIRCUITS	53
V.	CIRCUITS FOR A.V.C. AND MULTIPLE VALVES	63
VI.	THE OUTPUT STAGE	77
VII.	PUSH-PULL AMPLIFIERS	90
VIII.	POWER SUPPLY CIRCUITS	103
IX.	COMPLETE MODERN RADIO RECEIVER CIRCUITS	120
	INDEX	135